

## Schaltpläne mit dem Paket **circuitikz** erstellen

```
1 \begin{circuitikz}
2   \draw
3     (0,0) --(1,0) to [european resistor, l=$47\text{k}\Omega$] (3,0) --(5,0)
4       to [C, l=$470\mu\text{F}$] (7,0) -- (8,0)
5     (4.5,0) to [short, -*] (4.5,0) -- (4.5,-2)
6     (4.5,-2) -- (5,-2) to [voltmeter, l=$U_C$] (7,-2) -- (7.5,-2)
7     (7.5,-2) to [short, -*] (7.5,0)
8     (8,1) node[spdt, rotate=90] (Ums) {}
9     (Ums) node[right=0.4cm] {$WS$}
10    (Ums.out 1) node[left] {1}
11    (Ums.out 2) node[right] {2}
12    (0,0) |- (2,4) to [closing switch, l=$S$] (3,4) to [battery1, l=$U$]
13      (5,4) -| (Ums.out 2)
14    (Ums.in) -- (8,0)
15    (Ums.out 1) |- (0,2) to [short, -*] (0,2)
16  ;
17 \end{circuitikz}
```

---

